

Addis Ababa University
Addis Ababa Institute of Technology
Center of Information Technology and Scientific Computing
Department of Software Engineering
Course: Fundamentals of Electrical Circuits

Final -Exam for 1st Year 2nd Semester Software Engineering

Weight: 40 %

Time Allotted: 3.00 hrs.

Full Name: _____ **ID.No:** _____

Section: _____

Instructions: Please Read Carefully Before Proceeding.


- 1. Read all of the instruction and all of the question before beginning the exam*
- 2. This is a closed book, closed-notes examination.*
- 3. There are 11 questions and Two bonus in this exam, totaling 40 points*
- 4. On all the problems, please show your work clearly, to get full credit*
- 5. Non – programmable Calculators are allowed, but borrowing is not allowed*
- 6. Your mobile phones must be turned off during the exam*
- 7. Write your name and ID number on this page.*
- 8. Please attempt each of the question rather than leaving unanswered or blank.*
- 9. When you are told that time is up, please stop working on the test*
- 10. This exam contains 8 pages, including this one. Thus, you must check that everything is complete.**

Prepared By: Dr.Mani Sarma Vittapu.


Question	1	2	3	4	5	6	7	8	9	10	11
Maximum Marks	5	5	3	5	5	5	4	3	5	2	3
Earned Marks											
Total											

Good Luck!

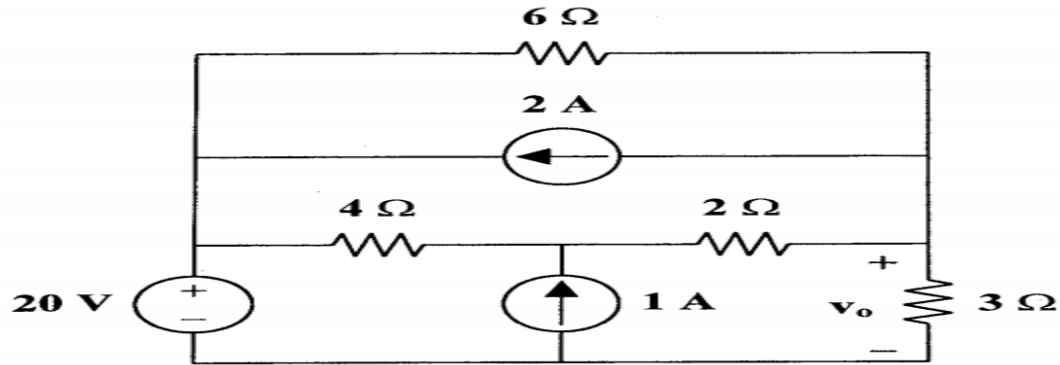
1. Apply **Superposition principle** to find **V_o** in the circuit given below.(5 points)



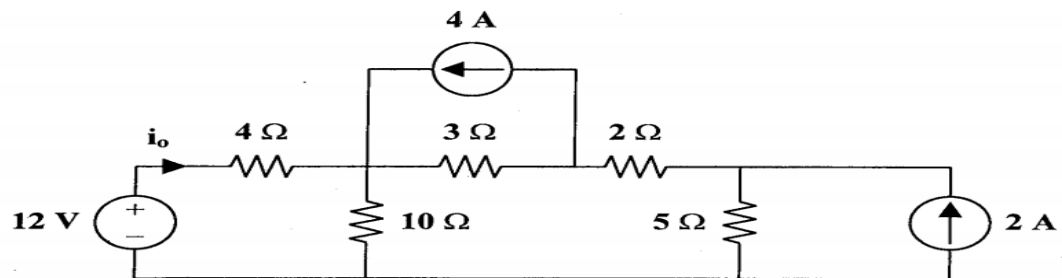
2. For the circuit given below find the **i_o** using **Source Transformation**.(5 points)



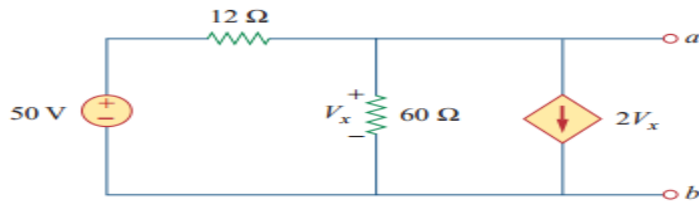
3. Obtain the Thevenin and Norton Equivalent circuits for the circuit given below seen from the a-b terminals.(3points)



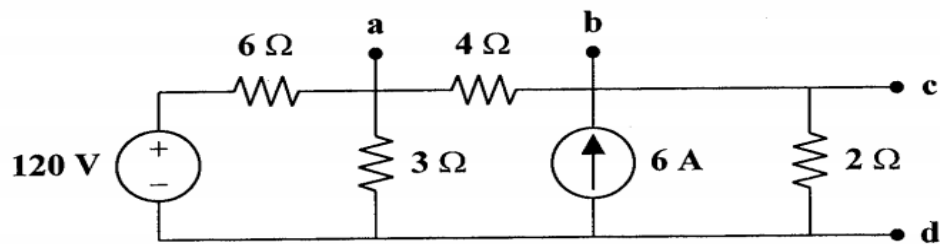
4. Obtain the Norton Equivalent when viewed from the terminals given (5 points)
A) a-b B) c-d



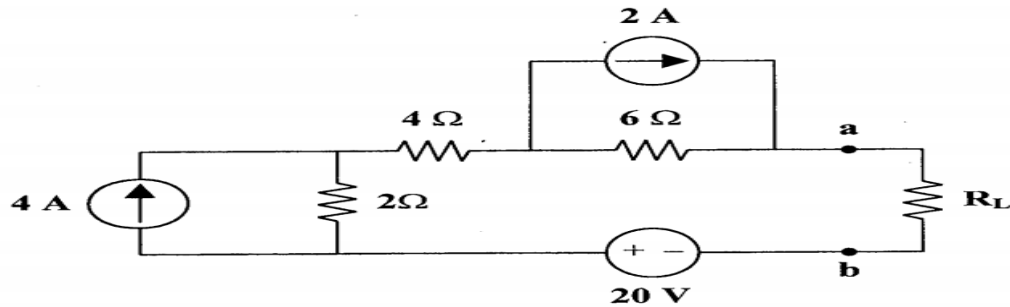
5. For the circuit given below (5 point)
- Obtain the Thevenin Equivalent(2 Points)
 - Calculate the current when $R_L=8\Omega$ (1 Point)
 - Find R_L for maximum power deliverable to R_L (1 point)
 - Determine the maximum power (1 Point)



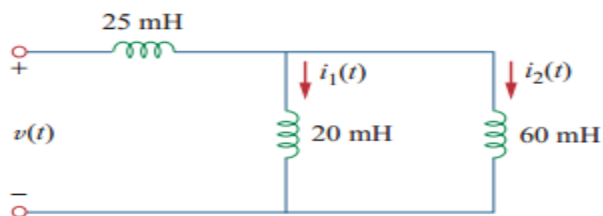6. Consider the following circuit with $v(t) = 12e^{-3t} \text{ mV}$ for $t > 0$ and $i_1(0) = -10 \text{ mA}$. Find (5 points).
- $i_2(0)$
 - $i_1(t)$
 - $i_2(t)$



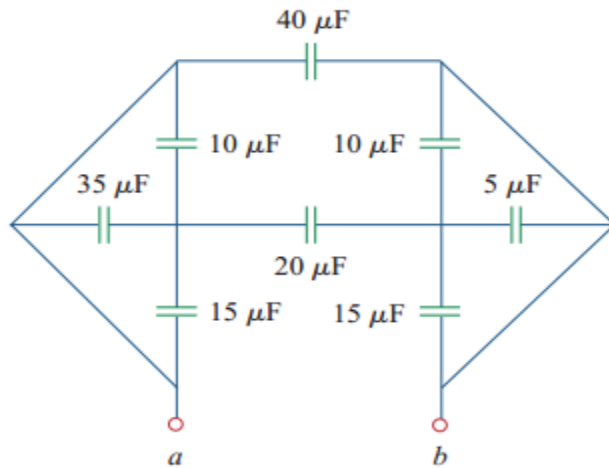
7. Find the equivalent Capacitance at the terminal a-b of the following circuit. (4 points)



8. Find the **amplitude**, **frequency**, and **phase angle** of each of the given sinusoids. (3 Points)
- $V(t) = -5\sin(10t-45)$
 - $I(t) = -2.5\cos(2\pi t)$

9. An RLC circuit with resistance ($R=20\Omega$), capacitance of ($C=20\text{mF}$) and inductance of ($L=20\text{mH}$) which are connected in series, is exposed to frequency of 50Hz , with peak voltage ($\mathcal{E}_m=100\text{V}$) source. Then, (5 points)
- What is the total impedance of the circuit?
 - What is the phase angle?
 - What is the power delivered? And the power factor?
 - How much capacitance be added to maximize the power in the circuit?

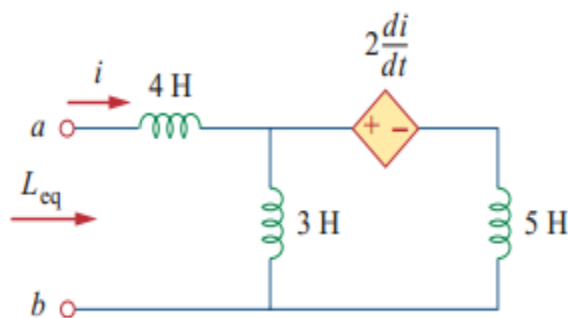10. (**Bonus**) Determine **L_{eq} (equivalent inductance)** that may be used to represent the inductive network (2 Points)



11. (Bonus) Explain generation of Sinusoidal wave? (3 points)

Problem: Find the **amplitude**, **frequency**, and **phase angle** of each of the given sinusoids.

c. $V(t) = -5\sin(10t-45)$

d. $I(t) = -2.5\cos(2\pi t)$